

BIOM1010: Engineering in Medicine and Biology


Tutorial: Computational Modelling in Bioengineering

Socrates Dokos

30 September 2018

Voltage Distribution in a Passive Neural Membrane

Steady-state passive electrical behaviour of an unmyelinated nerve cell axon of length $L = 10$ mm can be approximated by a thin cylinder of radius $r = 25 \mu\text{m}$, filled with axoplasmic medium of resistivity $\rho_i = 0.2 \Omega \text{ m}$, and surrounded by a membrane of resistance $r_m = 0.1 \Omega \text{ m}^2$. If a current of $I = 1 \mu\text{A}$ is injected into one end of the axon, and assuming the extracellular potential is set everywhere to ground, this system can be represented as N discrete circuit elements, each of length Δx , shown below:

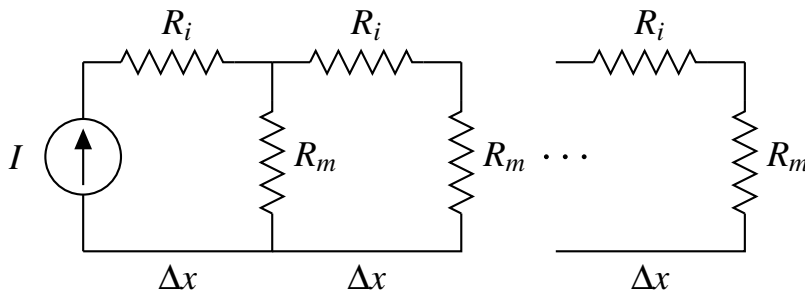


where the value of each R_i and R_m will depend on N according to

$$R_i = \frac{\rho_i \Delta x}{\pi r^2}, \quad R_m = \frac{r_m}{2\pi r \Delta x}, \quad \Delta x = \frac{L}{N-1}$$

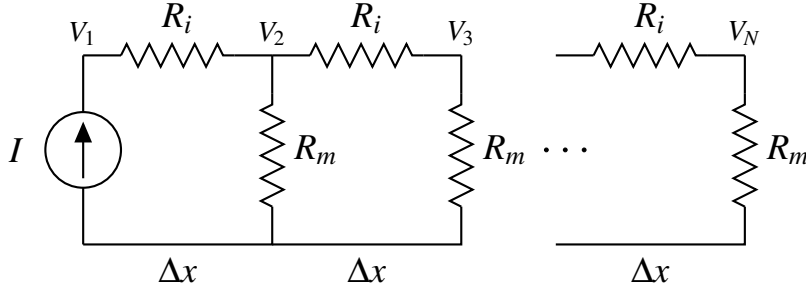1. Use MATLAB to solve and plot the membrane voltage V_m across the R_m 's as a function of length along the axon for $N = 200$. Note that V_m should monotonically decrease from the current source.
2. Plot the natural logarithm of V_m , i.e. $\ln(V_m)$, as a function of length along the first half of the axon (i.e. over the first 5 mm), and use MATLAB's curve fitting tools to determine the equation of the line of best fit.
3. Find the resulting equation representing V_m itself as a function of length along the first 5 mm of the axon.

Solution to 1

Label the membrane voltages at each node by $V_1, V_2, V_3, \dots, V_N$ as shown in the diagram below:



The total current flowing into each node horizontally (i.e. from the adjacent R_i 's) must equal the current flowing out of the node vertically through R_m . This is known as Kirchhoffs current law. For node k in general, Kirchhoffs current law can be written mathematically as:

$$\frac{V_{k-1} - V_k}{R_i} + \frac{V_{k+1} - V_k}{R_i} = \frac{V_k}{R_m}$$

which can be re-arranged to

$$\frac{V_{k-1}}{R_i} - \frac{2V_k}{R_i} + \frac{V_{k+1}}{R_i} = \frac{V_k}{R_m}$$

or

$$-\left(\frac{1}{R_i}\right)V_{k-1} + \left(\frac{2}{R_i} + \frac{1}{R_m}\right)V_k - \left(\frac{1}{R_i}\right)V_{k+1} = 0$$

The only exceptions are for nodes 1 and N . For node 1, we have:

$$\frac{V_2 - V_1}{R_i} = -I$$

or

$$\left(\frac{1}{R_i}\right)V_1 - \left(\frac{1}{R_i}\right)V_2 = I$$

For node N , we have:

$$\frac{V_{N-1} - V_N}{R_i} = \frac{V_N}{R_m}$$

or

$$\left(\frac{1}{R_i} + \frac{1}{R_m}\right)V_N - \left(\frac{1}{R_i}\right)V_{N-1} = I$$

Combining all the above equations, we can form the following matrix system of equations:

$$\begin{bmatrix} \frac{1}{R_i} & -\frac{1}{R_i} & 0 & \dots & 0 \\ -\frac{1}{R_i} & \left(\frac{1}{R_m} + \frac{2}{R_i}\right) & -\frac{1}{R_i} & \dots & 0 \\ \vdots & & \ddots & & \vdots \\ 0 & \dots & -\frac{1}{R_i} & \left(\frac{1}{R_m} + \frac{1}{R_i}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} I \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

The following MATLAB code generates this matrix system, $Av = b$ for $N = 200$, where v is the vector of membrane voltages, and solves for these:

```

N = 200;
A = zeros(N);           % initializes A to a NxN matrix of 0's
b = zeros(N,1);         % initializes b to a Nx1 column vector of 0's
b(1) = 1e-6;            % 1 uA

Delta_x = 0.01/(N-1);
Ri = 0.2*Delta_x/(pi*26e-6^2);
Rm = 0.1/(2*pi*25e-6*Delta_x);
A(1,1) = 1/Rm+1/Ri;
A(2,1) = -1/Ri;
A(N,N) = 1/Rm+1/Ri;
A(N,N-1) = -1/Ri;
for k = 2:N-1
    A(k,k) = 1/Rm+2/Ri;
    A(k,k-1) = -1/Ri;
    A(k,k+1) = -1/Ri;
end
Vm = A\b;
x = (0:Delta_x:0.01)*1000;
plot(x,1000*Vm,'k'), xlabel('length along axon (mm)'), ...
    ylabel('membrane voltage (mV)');

```

This code produces the following plot:

